

203-NYB-05  
Electricity and Magnetism  
Professor: Ernest Dubeau

AC Circuits: Lab 1  
By:  
Philippe Goulet

November 1, 2018  
Departement of Physics  
Champlain Regional College  
Lennoxville, Quebec, Canada

# Prelab

**1.1 An Oscilloscope is connected across a power source and the screen displays the image seen in figure.**

**a) What is the peak voltage of the signal (include the uncertainty)?**

$$20.0\text{V} \pm 0.5\text{V} \quad (1.1)$$

**b) What is the period of the signal (include the uncertainty)?**

$$0.100\text{s} \pm 0.005\text{s} \quad (1.2)$$

**c) What is the frequency of the power source (include the uncertainty)?**

$$\begin{aligned} f &= \frac{1}{T} \\ &= \frac{1}{0.100\text{s} \pm 0.005\text{s}} \\ &= 10.0\text{Hz} \pm 0.5\text{Hz} \end{aligned} \quad (1.3)$$

**d) If a DMM were to be connected across the same power source, what reading would you expect (Include the uncertainty)?**

$$\begin{aligned} \Delta V_{rms} &= \frac{\Delta V_{\max}}{\sqrt{2}} \\ &= \frac{20.0\text{V} \pm 0.5\text{V}}{\sqrt{2}} \\ &= 14.1\text{V} \pm 0.7\text{V} \end{aligned} \quad (1.4)$$

e) Write the sinusoidal function that represents the signal given off by the power source ( do not include the uncertainty)?

$$\begin{aligned}\sin(\omega t + \phi) &= \sin(2\pi f * t + \phi) \\ &= \sin(2\pi 10 * t + 0) \\ &= \sin(20\pi t)\end{aligned}\tag{1.5}$$

f) This power source is now connected to a single resistor with resistance  $R = (100 \pm 2)\Omega$ . What is the value of  $I_{\max}$  (include uncertainties)?

$$\begin{aligned}\Delta V_{\max} &= I_{\max} R \\ I_{\max} &= \frac{\Delta V_{\max}}{R} \\ I_{\max} &= \frac{20.0\text{V} \pm 0.5\text{V}}{(100 \pm 2)\Omega} \\ I_{\max} &= 200\text{mA} \pm 9\text{mA}\end{aligned}\tag{1.6}$$

g) How much current passes through this resistor at  $t = 0.0050\text{s}$  (no uncertainties)

$$\begin{aligned}I(t) &= \frac{\Delta V(t)}{R} \\ I(0.050) &= \frac{\Delta V(0.050)}{R} \\ &= \frac{0\text{V}}{100\Omega} \\ &= 0\end{aligned}\tag{1.7}$$

h) How much power ( on average ) is delivered to this resistor ( include uncertainties )?

$$\begin{aligned}P_{rms} &= \Delta V_{rms} I_{rms} \\ &= \frac{\Delta V_{\max}}{\sqrt{2}} \frac{I_{\max}}{\sqrt{2}} \\ &= \frac{20.0\text{V} \pm 0.5\text{V}}{\sqrt{2}} \frac{200\text{mA} \pm 9\text{mA}}{\sqrt{2}} \\ &= 3.17\text{W} \pm 0.38\text{W}\end{aligned}\tag{1.8}$$

i) How much current passes through this resistor at  $t = 0.025\text{s}$  (no uncertainties)

$$\begin{aligned} I(t) &= \frac{\Delta V(t)}{R} \\ I(0.025) &= \frac{\Delta V(0.025)}{R} \\ &= \frac{20\text{V}}{100\Omega} \\ &= 0.2\text{A} \end{aligned} \tag{1.9}$$

j) How much current passes through this resistor at  $t = 0.10\text{s}$  (no uncertainties)

$$\begin{aligned} I(t) &= \frac{\Delta V(t)}{R} \\ I(0.10) &= \frac{\Delta V(0.10)}{R} \\ &= \frac{0\text{V}}{100\Omega} \\ &= 0 \end{aligned} \tag{1.10}$$

## Aims

This lab was conceived to explore the basic concepts of AC circuits and observe and measure the properties of different components ( such as resistors, capacitors and inductors ) when exposed to alternating currents of various frequencies.

## Aparatus

- Oscilloscope
- Stopwatch
- Pasco Digital Function Generator (ac source)
- Digital Multimeter (*BK* and *Brunelle*)

- Lamp
- A 1 $\mu$ F capacitor

## AC circuit with a single resistor

### 4.1 Procedure

- Replicate the circuit shown in figure 11.
- Turn on both digital multimeters and set them to ac mode.
- Set the frequency of the AC source to 1000hz.
- Connect the lamp to the channel A of your oscilloscope using the coaxial cable. You should observe a sinusoidal pattern on the oscilloscope's screen.
- Adjust the amplitude of the AC source to have a  $\Delta V_{\max}$  of 4.0V as measured on the oscilloscope. Use this value of  $\Delta V_{\max}$  to calculate  $\Delta V_{rms}$ . Include the uncertainties.
- Draw a sketch of the oscilloscope screen and make sure to include a scale (and units).
- Use the Brunelle DMM to measure the *rms* voltage across the resistor (a lamp) and use the BK digital multimeter to measure the *rms* current (note uncertainties in both cases).
- Compare the  $\Delta V_{rms}$  measured with the digital multimeter to the  $\Delta V_{rms}$  calculated previously to verify whether or not the digital multimeter actually measures the *rms* voltage. Make sure to account for uncertainties.
- Use the AC readings of both digital multimeters and Ohm's law in AC (see theory) to calculate the resistance of the lamp (include uncertainties). Use the measure values of  $\Delta V$  and  $I_{rms}$  to determine the average power delivered to R (include uncertainties)
- Measure the period T of the signal on the oscilloscope's screen. Use this measured value to calculate the frequency and compare it to the frequency given by the AC power source. (include uncertainties).
- Change the frequency of the AC power source to 100 Hz.
- Adjust the time/div knob of the oscilloscope until you can clearly see the sinusoidal wave on the screen. Note down the new time scale used.

- Set the AC source to 10Hz and repeat the last step.
- Predict how many times the lamp would blink in 10 seconds if you set the frequency to 1Hz. Write down your prediction.
- Change the frequency of the AC source to 1Hz and verify your prediction.
- Turn off the AC source before performing the next step for safety.

## 4.2 Measurements

$$\Delta V_{\max} = 4.0V \pm 0.2V \quad (4.1)$$

$$\Delta V_{rms} = 2.79V \pm 0.06V \quad (4.2)$$

$$I_{rms} = 4.0V \pm 0.2V \quad (4.3)$$

$$T = 1.00ms \pm 0.04ms \quad (4.4)$$

## 4.3 Calculations

$$\begin{aligned} \Delta V_{rms} &= \frac{\Delta V_{\max}}{\sqrt{2}} \\ \Delta V_{rms} &= \frac{4.0V \pm 0.2V}{\sqrt{2}} \\ \Delta V_{rms} &= 2.8V \pm 0.1V \end{aligned} \quad (4.5)$$

$$\begin{aligned} P_{avg} &= \Delta V_{rms} I_{rms} \\ P_{avg} &= 2.79V \pm 0.06V * 4.0V \pm 0.2V \\ P_{avg} &= 0.285W \pm 0.012W \end{aligned} \quad (4.6)$$

$$\begin{aligned} F &= \frac{1}{T} \\ F &= \frac{1}{0.001s \pm 0.0004s} \\ F &= 1000Hz \pm 40Hz \end{aligned} \quad (4.7)$$

## 4.4 Discussion

The voltage<sub>rms</sub> measured at (4.2) agrees with the calculated value at (4.5)  
The frequency calculated at (4.7) agrees with the given value of 1000 Hz  
When the frequency was set to 100Hz, a time scale of 2ms/div was needed for proper observation

When the frequency was set to 10Hz, a time scale of 20ms/div was needed for proper observation. The sine wave shown on the oscilloscope also started flashing

Since this is an ac circuit, the lamp should flash twice per period. Thus, by setting the frequency to 1 Hz should make the lamp light up 20 times over 10 seconds. This was confirmed when tested, and the lamp does flash twice per period because there is two voltage peaks during one period.

## AC circuit with an inductor

### 5.1 Procedure

- Replace the lamp by a 10mH inductor.
- Set the frequency of the AC source to 1800 Hz
- Adjust the horizontal scale of the oscilloscope to see the sinusoidal pattern on the screen.
- Measure the value of  $\Delta V_{Lrms}$  and  $I_{Lrms}$ . Use these values to calculate  $X_L$  (include uncertainties and units on  $X_L$ ).
- Use the calculated value of  $X_L$  to calculate L with its uncertainties.
- Verify that the calculated value of L is in agreement with the nominal value of  $(10 \pm 1)\text{mH}$
- Now set frequency of the AC source to 1600 Hz. Observe how the reading of both digital multimeters change. Interpret the variation
- Turn off the AC source before performing the next step for safety.

#### 5.1.1 Measurements

With  $F=1800\text{Hz}$

$$\Delta V_{Lrms} = 2.73\text{V} \pm 0.06\text{V} \quad (5.1)$$

$$I_{rms} = 23.8\text{mA} \pm 0.8\text{mA} \quad (5.2)$$

With  $F=1600\text{Hz}$

$$\Delta V_{Lrms} = 2.73\text{V} \pm 0.06\text{V} \quad (5.3)$$

$$I_{rms} = 26.4\text{mA} \pm 0.8\text{mA} \quad (5.4)$$

### 5.1.2 Calculations

$$\begin{aligned}\Delta V_{Lrms} &= X_L I_{rms} \\ X_L &= \frac{\Delta V_{Lrms}}{I_{rms}} \\ X_L &= \frac{2.73V \pm 0.06V}{23.8mA \pm 0.8mA} \\ X_L &= 11.47 \frac{V}{A} \pm 0.29 \frac{V}{A}\end{aligned}\tag{5.5}$$

$$\begin{aligned}X_L &= \omega L \\ L &= \frac{X_L}{\omega} \\ L &= \frac{114.7 \frac{V}{A} \pm 0.3 \frac{V}{A}}{2\pi 1800Hz} \\ L &= 10.14mH \pm 0.26mH\end{aligned}\tag{5.6}$$

### 5.1.3 Discussion

The value of L calculated at (5.6) agrees with the nominal value of  $10mH \pm 1mH$ . When the frequency of the AC source was changed to 1600Hz the  $\Delta V_{Lrms}$  did not change and the  $I_{rms}$  went down linearly.

## AC Circuit with a capacitor

### 6.1 Procedure

- Replace the inductor by a  $1.0\mu F$  capacitor and set the frequency of the AC source to 1000Hz
- Measure the  $\Delta V_{Crms}$  and  $I_{Crms}$  using both digital multimeters.
- Calculate  $X_C$  using these measurements (ignore uncertainties).
- Use the calculated  $X_C$  to determine C (ignore uncertainties).
- Calculate the percent error on C.
- Predict the value of  $I_{Crms}$  when the frequency of the



## 6.2 Measurements

$$\Delta V_{Crms} = 2.76V \quad (6.1)$$

$$I_{Crms} = 16.8mA \quad (6.2)$$

$$I_{Crms(600hz)} = 10.1mA \quad (6.3)$$

## 6.3 Calculations

$$\begin{aligned} \Delta V_{Crms} &= X_L I_{Crms} \\ X_C &= \frac{\Delta V_{Crms}}{I_{Crms}} \\ X_C &= \frac{2.76V}{16.8mA} \\ X_C &= 164.3 \frac{V}{A} \end{aligned} \quad (6.4)$$

$$\begin{aligned} X_C &= \frac{1}{\omega C} \\ C &= \frac{1}{\omega X_C} \\ C &= \frac{1}{2\pi 1000Hz * 164.3 \frac{V}{A}} \\ C &= 0.9687\mu F \end{aligned} \quad (6.5)$$

$$\begin{aligned} \%error &= 100 * (C_{cal} - 1.00\mu F) / 1.00\mu F \\ \%error &= 100 * (0.9687\mu F - 1.00\mu F) / 1.00\mu F \\ \%error &= 3.13\% \end{aligned} \quad (6.6)$$

$$\begin{aligned} \Delta V_{Crms} &= X_L I_{Crms} \\ I_{Crms} &= \frac{\Delta V_{Crms}}{X_L} \\ I_{Crms} &= \frac{2.76V}{\frac{1}{2\pi * 600Hz * 1.00\mu F}} \\ I_{Crms} &= 10.4mA \end{aligned} \quad (6.7)$$

## 6.4 Discussion

I predicted that the current would go down to 10.4mA as calculated in(6.7). However, the measured  $I_{Crms}$  went down to 10.1mA. A logical explanation

for this would be that I wrongly assumed the voltage would stay identical, but since I have control of the source, I don't believe that to be correct. A 3% difference could've been explained by uncertainties in both the calculation and the measurement.